

| | | | | | |
|--------------------|--------|--|--------|----------|----------|
| U 237 B,BG | LIN-IC | LED-Band-Anst./driver (5LEDs, lin.) | 8-DIP | - | |
| U 244 B | LIN-IC | LED-Band-Anst./driver (5 LEDs, lin.) | 8-DIP | - | |
| U 247 B,BG | LIN-IC | Erweit./extension f.U237(=5+5LEDs) | 8-DIP | - | |
| U 250 B | LIN-IC | IR-Empf.-Verst./receiver amplifier | 16-DIP | - | |
| U 252 B | LIN-IC | VC-Breitbandverst./wide band amplif. | 8-DIP | - | |
| U 254 B | LIN-IC | Erweit./extension f.U244(=5+5LEDs) | 8-DIP | - | |
| U 257 B,BG | LIN-IC | =U 237 B: log. | 8-DIP | - | |
| U 263 B1,B2 | LIN-IC | Triac-Nullspg.-Sch./zero cross. sw. | 8-DIP | - | |
| U 264 B | LIN-IC | TV-Tuner-Frequ.-Teiler/divider, 1GHz | 8-DIP | - | |
| U 265 B | LIN-IC | TV-UHF-Frequenzteiler/divider | 8-DIP | - | |
| U 266 B | LIN-IC | TV-UHF-Frequenzteiler/divider | 8-DIP | - | |
| U 267 B,BG | LIN-IC | =U 247: log. | 8-DIP | - | |
| U 317 | MOS-IC | IR-FB Empf./receiver | 28-DIP | - | |
| U 318 M | MOS-IC | IR-FB Empf./receiver | 28-DIP | - | |
| U 321 M | MOS-IC | IR-FB Sender/transmitter | 18-DIP | - | |
| U 327 M | MOS-IC | IR-FB Sender/transmitter | 24-DIP | - | |
| U 328 M | MOS-IC | IR-FB Sender/transmitter | 24-DIP | - | |
| U 329 M | MOS-IC | IR-FB Sender/transmitter | 28-DIP | - | |
| U 334 M | MOS-IC | TV, FB PCM-Empfänger/receiver | 28-DIP | - | |
| U 336 M | MOS-IC | TV, FB PCM-Empfänger/receiver | 28-DIP | - | |
| U 337 M | MOS-IC | TV, FB PCM-Empfänger/receiver | 16-DIP | - | |
| U 338 M | MOS-IC | TV, FB PCM-Empfänger/receiver | 8-DIP | - | |
| U 344 M | MOS-IC | FB-Empfänger/receiver | - | - | |
| U 348 M | MOS-IC | IR-FB PCM-Empfänger/receiver | 8-DIP | - | |
| U 401 B,BR | LIN-IC | Recorder HIGH COM System (nur als Modul lfb./only adjusted kit) | 24-DIP | - | |
| U 407 B | LIN-IC | Recorder HIGH COM System | 24-DIP | - | |
| U 408 B | LIN-IC | Recorder-Componder | 20-DIP | - | |
| U 420 | Si-Di | =MUR 420 (Typ-Code/Stempel/markung) | 31 | - | →MUR 420 |
| U 460 | Si-Di | =MUR 460 (Typ-Code/Stempel/markung) | 31 | - | →MUR 460 |
| U 465 B | LIN-IC | =U 265B: invert.Ein-Ausg./inp.-outp. | 8-DIP | - | |
| U 664 B,BS,BSH | LIN-IC | GHz Frequenzteiler/divider, 1:64 | 8-DIP | - | ** |
| U 665 B | LIN-IC | GHz Frequ.-Teiler/divider, 1:960/1024 | 8-DIP | - | ** |
| U 710 D | MOS-IC | Sensor f. 8 Tasten/keys | 16-DIP | - | ** |
| U 711 D | MOS-IC | Decoder f. U 710D | 16-DIP | - | ** |
| U 806 D | MOS-IC | IR-FB Empfänger/receiver | 24-DIP | - | |
| U 807 D | MOS-IC | IR-FB Sender/transmitter | 24-DIP | SAB 3021 | 24-DIP * |
| U 810 BS | LIN-IC | 1,2GHz Frequ.-Teiler/divider, 1:64 | 25 | - | |
| U 811 BS | LIN-IC | 1,2GHz Frequ.-Teiler/divider, 1:128 | 25 | - | |
| U 812 BS | LIN-IC | 1,2GHz Frequ.-Teiler/divider, 1:256 | 25 | - | |
| U 813 BS,BSE | LIN-IC | 1,1GHz F.-Teiler/divider, 1:64/128/256 | 8-DIP | - | |
| U 813 BS-FP,BSE-FP | LIN-IC | =U 813BS,BSE: SMD | 8-MDIP | - | |
| U 813 BS-SP,BSE-SP | LIN-IC | =U 813BS,BSE:Fig. → | 6-SIP | - | |
| U 820 B | LIN-IC | NF-E, 16V, 1.1W(9V/8Ω) | 8-DIP | - | ** |
| U 821 B | LIN-IC | NF-E, 16V, 1W(9V/8Ω) | 8-DIP | - | ** |
| U 822 BS | LIN-IC | 2,2GHz Frequ.-Teiler/divider, 1:2 | 25 | - | |
| U 824 BS | LIN-IC | =U 822BS: 1:4 | 25 | - | |
| U 826 B,BS | LIN-IC | TV, Stereo-Ton-ZF, Dem | 8-DIP | - | ** |
| U 828 B | LIN-IC | TV, Stereo-Ton-ZF, Dem | 8-DIP | - | |
| U 829 B,BS | LIN-IC | TV, Stereo-Ton-Demodulator | 8-DIP | - | |
| U 833 BS,BSE | LIN-IC | =U 813BS,BSE: 1,3GHz | 8-DIP | - | |
| U 833 BS-FP,BSE-FP | LIN-IC | =U 813BS,BSE: 1,3GHz | 8-MDIP | - | |
| U 833 BS-SP,BSE-SP | LIN-IC | =U 813BS,BSE: 1,3GHz | 6-SIP | - | |
| U 836 BS | LIN-IC | 1,3GHz Frequ.-Teiler/divider, 1:256 | 8-DIP | - | ** |
| U 842 BS | LIN-IC | 2,3GHz Frequ.-Teiler/divider, 1:2 | 25 | - | ** |
| U 844 BS | LIN-IC | =U 842BS: 1:4 | 25 | - | ** |