# AUTOMOTIVE AND HOUSEHOLD SECURITY SIREN DRIVER

**ISSUE 8 – JUNE 2007** 

FEATURES

#### INTRODUCTION

The ZSD100 is a frequency swept alarm signal generator designed specifically for static and automotive security alarm systems. One ZSD100, two timing capacitors, an in-expensive TO92 darlington, piezo transducer and coupling transformer is all that is necessary to produce an ear piercing 120 dB alarm siren.


Including an audio frequency signal generator, low frequency sweep generator, disable circuitry and output driver stages, the ZSD100 provides every function necessary to produce a standard alarm signal. Available in an 8 pin SO package, the IC gives a low cost compact solution to siren signal generation. The device operates from supplies of 4V up to 18V and is ideal for security alarms in battery powered applications, burglar alarms and automotive anti theft systems.

- 4-18V Operating voltage range.
- Small external component count.
- Direct drive of darlington, mosfet and IGBT output stages.

**ZSD100** 

- Single ended or push-pull output stages.
- Suitable for automotive and static alarm systems.
- Low supply current 10mA operating
   1μA sleep mode
- Low cost 8 pin SO package.
- User selected audio and sweep frequencies.
- -40°C to 125°C operating temperature range.
- Choice of modulation waveform.


#### SCHEMATIC DIAGRAM

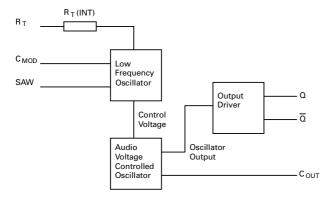


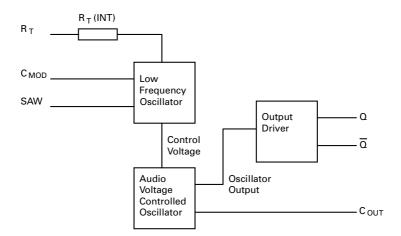
### **FUNCTIONAL DESCRIPTION**

The audio signal of the ZSD100 is generated using a squarewave oscillator whose output is capable of directly driving a wide range of output circuits. To produce a characteristic alarm siren sound, the frequency of the audio oscillator is swept over a fixed 2:1 range by a second, low frequency oscillator. The frequencies of both oscillators are controlled by  $R_T(INT)$  and capacitors  $C_{MOD}$  and  $C_{OUT}$ .



#### PIN DESCRIPTIONS

- R<sub>T</sub> Optional external resistor for improved frequency control. An external resistor improves the control of both the modulating and output oscillators.
  - The  $R_T$  pin is also used to power the device down. Either connecting  $R_T$  to  $V_{CC}$  or an open circuit will result in the device being disabled.
- SAW Selection of modulation waveform is made using the SAW pin. An open circuit
  produces a triangle wave, sawtooth is achieved by connecting SAW to the C<sub>MOD</sub>
  pin.
- 3.  $C_{MOD}$  An external capacitor is used to program the low frequency modulating oscillator. The value of  $C_{MOD}$  recommended is between  $0.1\mu F$  and  $100\mu F$ .
- G<sub>ND</sub>
- 5. C<sub>OUT</sub> An external capacitor is used to program the output oscillator. The value of C<sub>OUT</sub> recommended is between 1nF and 100nF.
- 6. Q Non inverted output driver
- 7. Q Inverted output driver
- 8. Vcc

### **ABSOLUTE MAXIMUM RATING**

### Power Dissipation (Tamb=25°C)

-0.5V to +20V  $V_{cc}$ **SO8** 

625mW Operating Temperature -40 to 125°C -65 to 150°C

Storage Temperature **ELECTRICAL CHARACTERISTICS** 

## TEST CONDITIONS (Unless otherwise stated):T<sub>amb</sub>=25°C, V<sub>CC</sub>=12V

			· an		
PARAMETER	SYMBOL	MIN.	TYP.	MAX.	CONDITIONS.
Supply Voltage Operating Range	Vcc	4V		18V	
Supply Current Disabled Enabled	Icc			1μΑ 25mA	R <sub>T</sub> O/C <u>,</u> V <sub>CC</sub> =18V R <sub>T</sub> , Q, Q at Gnd, V <sub>CC</sub> =18V
Modulating Oscillator Frequency Range	F <sub>MOD</sub>	0.1Hz		10Hz	V <sub>CC</sub> =4 to 18V
Frequency Value See Note 1	F <sub>MOD</sub>	3.3Hz 5.1Hz	4.3Hz 5.5Hz	5.4Hz 5.9Hz	R <sub>T</sub> =0, C <sub>MOD</sub> =10μF R <sub>T</sub> =470kΩ, C <sub>MOD</sub> =1μF
Output Oscillator Frequency Range	F <sub>OUT</sub>	100Hz		10kHz	V <sub>CC</sub> =4 to 18V
Centre Frequency (Note 2) Deviation Duty Cycle	F <sub>OUT</sub> ΔF <sub>OUT</sub>	1.01kHz	1.26kHz ±33% 49%	1.58kHz 55%	R <sub>T</sub> =0, C <sub>OUT</sub> =22nF
Output Source Current Sink Current Open Circuit Voltage	Isource Isink Vout(High) Vout(Low)	5mA 0.5mA V <sub>CC</sub> -1.5V		0.5V	V <sub>OUT</sub> =1.4V V <sub>OUT</sub> =1.4V I <sub>OUT</sub> =100μA I <sub>SINK</sub> =0.1μA
Frequency Control Components Internal Resistor External Resistor Modulation Capacitor Output Capacitor	R <sub>T</sub> (INT) R <sub>T</sub> (EXT) C <sub>MOD</sub> C <sub>OUT</sub>	0 0.1μF 1nF	61.5kΩ	1MΩ 100μF 100nF	


2850  $F_{MOD} = \frac{2000}{C_{MOD}(61.5 + R_T (EXT))}$ Note 1.

1710


Note 2.  $C_{OUT}$  in  $\mu F,\,R_T$  (EXT) in  $k\Omega$  $F_{OUT} = \frac{1710}{C_{OUT}(61.5 + R_T (EXT))} Hz$ 


 $C_{MOD}$  in  $\mu F$ ,  $R_T$  (EXT) in  $k\Omega$ 

### **TYPICAL CHARACTERISTICS**

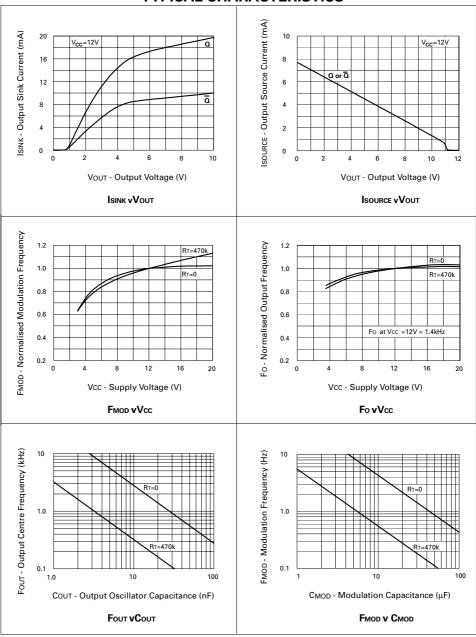


### **TYPICAL CHARACTERISTICS**

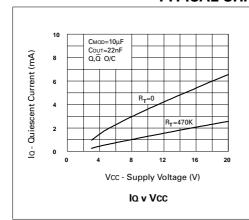

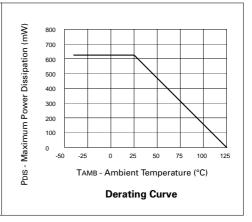


### **APPLICATIONS CIRCUITS**

### Piezo Sounder

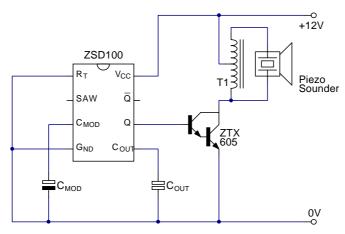

Utilizing a standard autotransformer driven piezo sounder, this circuit indicates a minimum component count alarm solution. In this configuration a ZTX605 darlington transistor can be connected directly to the ouput of the IC without the need for base resistors.


### Moving Coil Loudspeaker Sounder

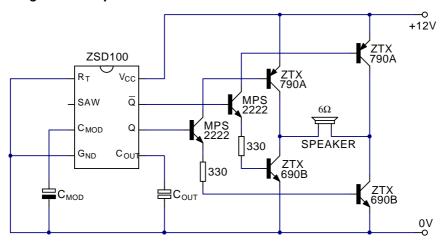

Moving coil loudspeakers are often used for the very highest output automotive alarm sounders. The ZSD100 complementary outputs, with the selection of ZTX790A and ZTX690B transistors, can drive this H bridge ouput circuit without any additional interface components.

Issue 8 - June 2007 www.zetex.com

### **Improved Frequency Control**

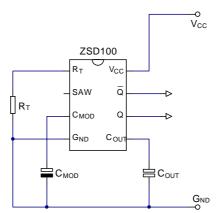


Improved frequency control can be achieved with an external resistor between the  $R_T$  pin and  $G_{ND}$ . An external resistor reduces the value of the timing capacitors required for the selected operating frequency and also reduces the ZSD100's power consumption.

**Note**: The outputs of the ZSD100 have been designed to avoid cross-conduction in full bridge output circuits. Large value external timing resistors can lead to a small level of cross-conduction. It is recommended that external timing resistors are not used with bridge output circuits.

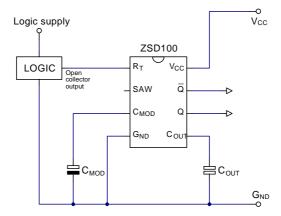
### **Remote Switching**

If the R<sub>T</sub> pin is switched open-circuit, all internal functions of the IC are shut down.



**Note:** A small leakage current in the open collector logic controller will enable the IC. If such leakage cannot be eliminated, its effect can be easily negated by adding a high value resistor (eg. 100k) between pin  $R_T$  and  $V_{CC}$ . This resistor will have no effect on frequency control.

Issue 8 - June 2007 www.zetex.com

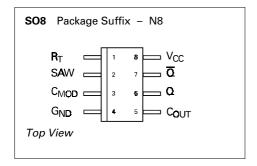

Part Number	Package	Part Mark
ZSD100N8	SO8	ZSD100

### Europe Zetex GmbH

Kustermann-Park Balanstraße 59 81541 München, Germany

Telefon: (49) 89 45 49 49 0 Fax: (49) 89 45 49 49 49 europe.sales@zetex.com

#### **Americas**

Zetex Inc 700 Veterans Memorial Highway Hauppauge, NY 11788 USA

Telephone: (1) 631 360 2222 Fax: (1) 631 360 8222

usa.sales@zetex.com

#### Asia Pacific

Zetex (Asia Ltd) 3701-04 Metroplaza Tower 1 Hing Fong Road, Kwai Fong Hong Kong

Fax: (852) 24250 494 asia.sales@zetex.com

Telephone: (852) 26100 611

### **Corporate Headquarters**

Zetex Semiconductors plc Zetex Technology Park, Chadderton Oldham, OL9 9LL United Kingdom

Telephone: (44) 161 622 4444 Fax: (44) 161 622 4446

hq@zetex.com

#### For international sales offices visit www.zetex.com/offices

Zetex products are distributed worldwide. For details, see www.zetex.com/salesnetwork

This publication is issued to provide outline information only which (unless agreed by the company in writing) may not be used, applied or reproduced for any purpose or form part of any order or contact or be regarded as a representation relating to the products or services concerned. The company reserves the right to alter without notice the specification, design, price or conditions of supply of any product or service.

Issue 8 - June 2007 www.zetex.com